#### **ENHANCED HIGH-SIDE CURRENT MONITOR**

#### **DESCRIPTION**

The ZXCT1010 is a high side current sense monitor. Using this device eliminates the need to disrupt the ground plane when sensing a load current.

It is an enhanced version of the ZXCT1009 offering reduced typical output offset and improved accuracy at low sense voltage.

The wide input voltage range of 20V down to as low as 2.5V make it suitable for a range of applications. A minimum operating current of just 4 $\mu$ A, combined with its SOT23-5 package make suitable for portable battery equipment.


#### **FEATURES**

- · Low cost, accurate high-side current sensing.
- · Output voltage scaling.
- Up to 2.5V sense voltage.
- 2.5V 20V supply range.
- 300nA typical offset current.
- 3.5µA quiescent current.
- 1% typical accuracy.
- SOT23 -5 package.

#### **APPLICATIONS**

- Battery Chargers
- Smart Battery Packs
- DC Motor control
- Over current monitor
- Power Management
- · Level translating
- Programmable current source

#### **APPLICATION CIRCUIT**

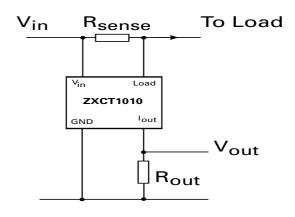

### ORDERING INFORMATION

PART NUMBER	PACKAGE	PARTMARKING
ZXCT1010E5	SOT23-5	1010



### **ABSOLUTE MAXIMUM RATINGS**

-0.6V to 20V (relative to GND) Voltage on any pin

Continuous output current 25mA

 $V_{in} + 0.5V > V_{sense}^{\dagger} > V_{in} - 5V$ Continuous sense voltage

-40 to 85°C Operating Temperature Storage Temperature -55 to 125°C Package Power Dissipation  $(T_A = 25^{\circ}C)$ 500mW SOT23-5

## **ELECTRICAL CHARACTERISTICS**

Test Conditions  $T_A$  = 25°C,  $V_{in}$  = 5V,  $R_{out}$  = 100 $\Omega$ .


SYMBOL	PARAMETER	CONDITIONS	LIMITS			UNIT
			Min	Тур	Max	
V <sub>in</sub>	V <sub>CC</sub> Range		2.5		20	V
I <sub>out</sub> 1	Output current	V <sub>sense</sub> = 0V	0	0.3	10	μA
		V <sub>sense</sub> = 10mV	85	100	115	μA
		V <sub>sense</sub> = 100mV	0.975	1.00	1.025	mA
		V <sub>sense</sub> = 200mV	1.95	2.00	2.05	mA
		V <sub>sense</sub> = 1V	9.7	10.0	10.3	mA
Iq	Ground pin current	V <sub>sense</sub> = 0V		3.5	8	μА
V <sub>sense</sub> 2	Sense Voltage		0		2500	mV
I <sub>sense</sub>	Load pin				100	nA
	input current					
Acc	Accuracy	$R_{\text{sense}} = 0.1\Omega$				
		V <sub>sense</sub> = 200mV	-2.5		2.5	%
Gm	Transconductance,			10000		μ <b>A</b> /V
	I <sub>out</sub> / V <sub>sense</sub>					
BW	Bandwidth	RF P <sub>in</sub> = -20dBm <sup>3</sup>		000		T
		$V_{\text{sense}} = 10\text{mV dc}$		300		kHz
		V <sub>sense</sub> = 100mV dc		2		MHz

<sup>&</sup>lt;sup>1</sup> Includes input offset voltage contribution



 $<sup>^{2}</sup>$ V<sub>sense</sub>=V<sub>in</sub>-V<sub>load</sub>  $^{3}$  -20dBm=63mVp-p into 50Ω

## **TYPICAL CHARACTERISTICS**

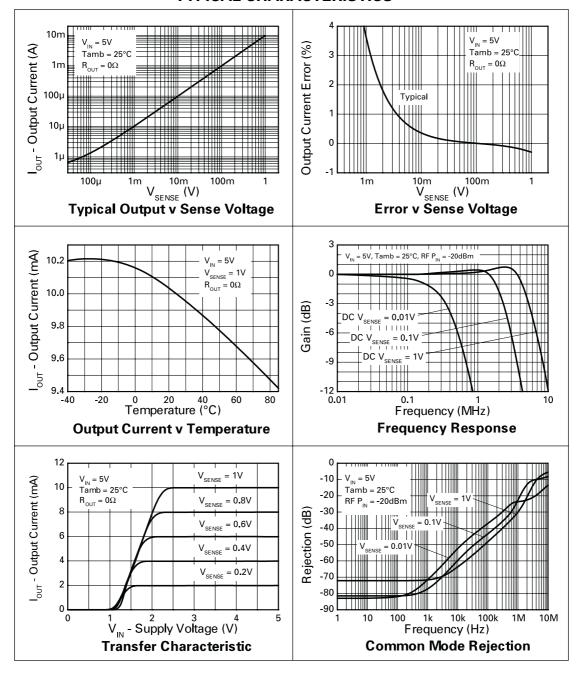





### PIN DESCRIPTION

Pin Name	Pin Function
V <sub>in</sub>	Supply Voltage
Load	Connection to load/battery
l <sub>out</sub>	Output current, proportional to V <sub>in</sub> -V <sub>load</sub>
GND	Ground

### **CONNECTION DIAGRAM**

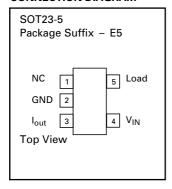

### **SCHEMATIC DIAGRAM**

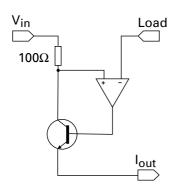




#### **POWER DISSIPATION**

The maximum allowable power dissipation of the device for normal operation (Pmax), is a function of the package junction to ambient thermal resistance ( $\theta$ ja), maximum junction temperature (Tjmax), and ambient temperature (Tamb), according to the expression:

$$P_{max} = (Tj_{max} - T_{amb}) / \theta_{ja}$$

The device power dissipation,  $P_{\text{D}}$  is given by the expression:

 $P_{D}=I_{out}.(V_{in}-V_{out})$  Watts

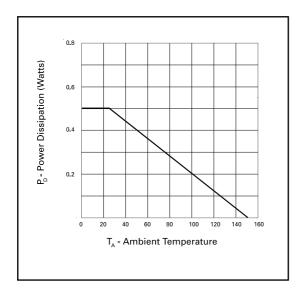

#### APPLICATIONS INFORMATION

The following lines describe how to scale a load current to an output voltage.

$$V_{sense} = V_{in} - V_{load}$$
 $V_{out} = 0.01 \times V_{sense} \times R_{out}^{1}$ 

E.g.

A 1A current is to be represented by a 100mV output voltage:

1)Choose the value of  $R_{sense}$  to give  $50mV > V_{sense} > 500mV$  at full load.


For example  $V_{sense} = 100 mV$  at 1.0A.  $R_{sense} = 0.1/1.0 => 0.1$  ohms.

2)Choose  $R_{out}$  to give  $V_{out}$  = 100mV, when  $V_{sense}$  = 100mV.

Rearranging <sup>1</sup> for  $R_{out}$  gives:  $R_{out} = V_{out} / (V_{sense} \times 0.01)$ 

 $R_{out} = 0.1 / (0.1 \times 0.01) = 100 \Omega$ 


### TYPICAL CIRCUIT APPLICATION

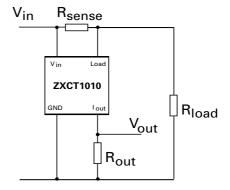

Where  $R_{load}$  represents any load including DC motors, a charging battery or further circuitry that requires monitoring,  $R_{sense}$  can be selected on specific requirements of accuracy, size and power rating.


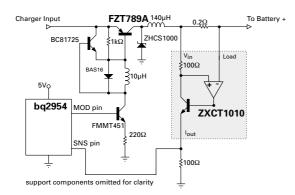
#### **APPLICATIONS INFORMATION (Continued)**




#### Li-Ion Charger Circuit

The above figure shows the ZXCT1010 supporting the Benchmarq bq2954 Charge Management IC. Most of the support components for the bq2954 are omitted for clarity. This design also uses the Zetex FZT789A high current Super- $\beta$  PNP as the switching transistor in the DC-DC step down converter and the FMMT451 as the drive NPN for the FZT789A. The circuit can be configured to charge up to four Li-lon cells at a charge current of 1.25A. Charge can be terminated on maximum voltage, selectable minimum current, or maximum time out. Switching frequency of the PWM loop is approximately 120kHz.
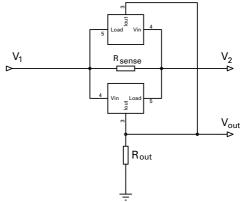
#### **Bi-Directional Current Sensing**


The ZXCT1010 can be used to measure current bi-directionally, if two devices are connected as shown below.



If the voltage V1 is positive with respect to the voltage V2 the lower device will be active, delivering a proportional output current to Rout. Due to the polarity of the voltage across Rsense, the upper device will be inactive and will not contribute to the current delivered to Rout. When V2 is more positive than V1, current will be flowing in the opposite direction, causing the upper device to be active instead.

Non-linearity will be apparent at small values of Vsense due to offset current contribution. Devices can use separate output resistors if the current direction is to be monitored independently.
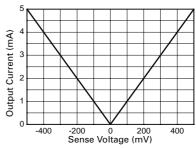
#### **Bi-directional Transfer Function**



Output Current v Sense Voltage




#### **APPLICATIONS INFORMATION (Continued)**

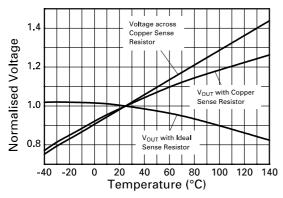
# PCB trace shunt resistor for low cost solution.

The figure below shows output characteristics of the device when using a PCB resistive trace for a low cost solution in replacement for a conventional shunt resistor. The graph shows the linear rise in voltage across the resistor due to the PTC of the material and demonstrates how this rise in resistance value over temperature compensates for the NTC of the device.


The figure opposite shows a PCB layout suggestion. The resistor section is 25mm x 0.25mm giving approximately  $150m\Omega$  using 1oz copper. The data for the normalised graph was obtained using a 1A load current and a  $100\Omega$  output resistor. An electronic version of the PCB layout is available at www.zetex.com/isense



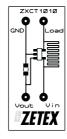Effect of Sense Resistor Material on Temperature Performance




Actual Size

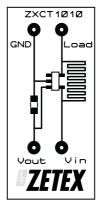

Layout shows area of shunt resistor compared to SOT23-5 package. Not actual size



## **PACKAGE DIMENSIONS SOT23-5**

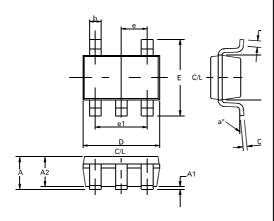

DIM	Millimetres		Inches		
	MIN	мах	MIN	мах	
А	0.90	1.45	0.035	0.057	
A1	0.00	0.15	0.00	0.006	
A2	0.90	1.3	0.035	0.051	
b	0.35	0.50	0.014	0.020	
С	0.09	0.20	0.0035	0.008	
D	2.80	3.00	0.110	0.118	
E	2.60	3.00	0.102	0.118	
E1	1.50	1.75	0.059	0.069	
е	0.95 REF		0.037 REF		
e1	1.90 REF		0.075 REF		
L	0.10	0.60	0.004	0.024	
a°	0	10	0	10	

#### © Zetex plc 2003

Zetex plc Fields New Road Chadderton Oldham, OL9 8NP United Kingdom Telephone (44) 161 622 4422 Fax: (44) 161 622 4446

Zetex GmbH Streitfeldstraße 19 D-81673 München

Germany Telefon: (49) 89 45 49 49 0 Fax: (49) 89 45 49 49 49 Zetex Inc Suite 315 700 Veterans Memorial Highway Hauppauge, NY 11788 USA

Telephone: (631) 360 2222 Fax: (631) 360 8222 Zetex (Asia) Ltd 3701-04 Metroplaza, Tower 1 Hing Fong Road Kwai Fong Hong Kong Telephone: (852) 26100 611 Fax: (852) 24250 494

These offices are supported by agents and distributors in major countries world-wide.

This publication is issued to provide outline information only which (unless agreed by the Company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned. The Company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.

For the latest product information, log on to  $\boldsymbol{www.zetex.com}$ 



**ISSUE 5 - MARCH 2003**